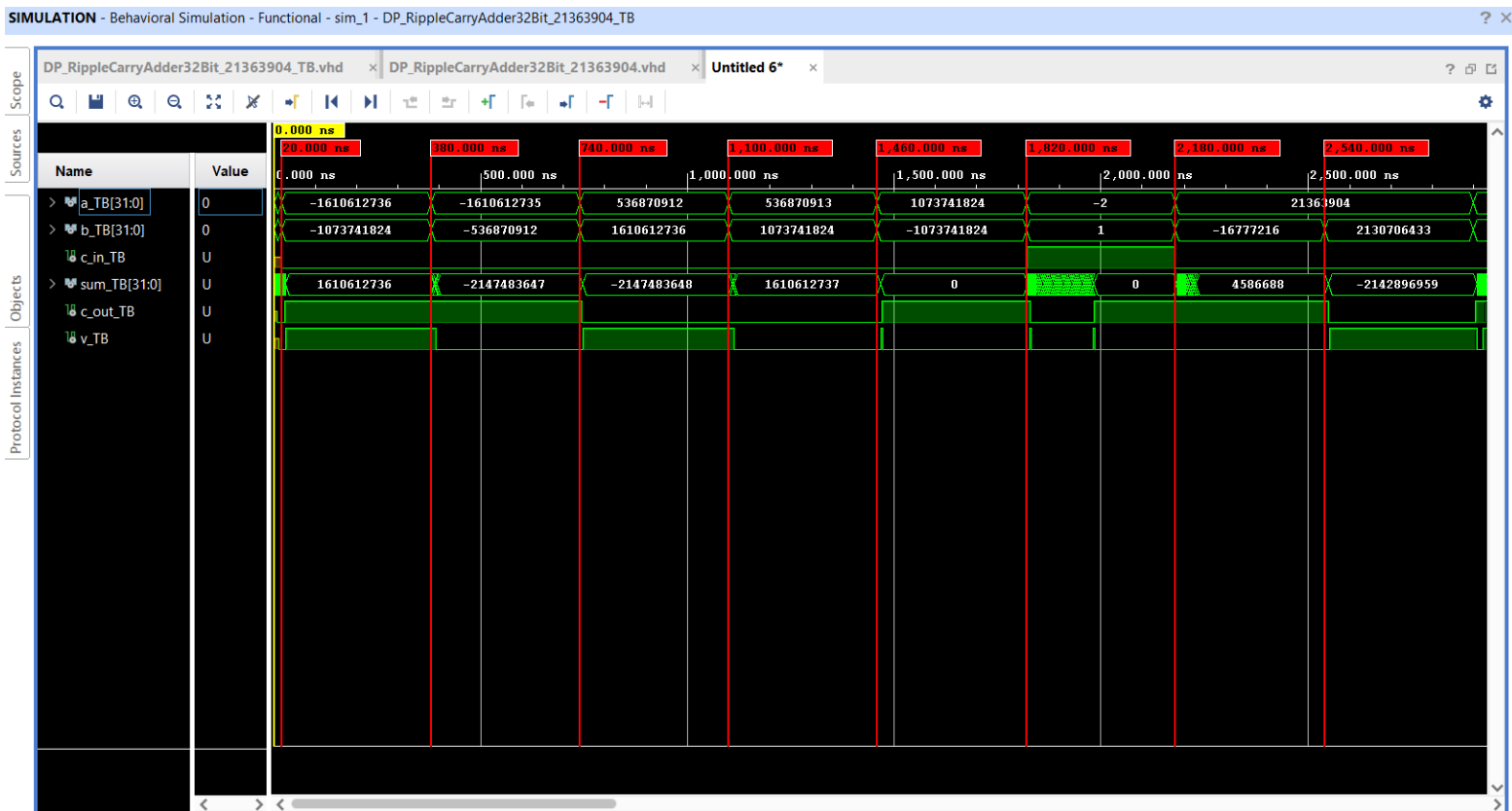



DP_ArithmeticLogicUnit_21363904




The timing diagram for the Ripple Carry Adder is shown above. On the following pages each of the eight cases are split up so we can see the propagation delay for each. All numbers are in Signed Decimal notation. In the above waveform, the **red lines** mark when the inputs change and a new test case is performed. In the images below the **yellow lines** mark when the correct value appears at *SUM*, after the propagation delay. Case 6 shows the worst case propagation delay (163ns for the correct result at *SUM*, plus another 4ns for the correct *C_{OUT}* and overflow). Cases 7 and 8 demonstrate adding numbers to my Student ID (21363904) to set the C Flag and V Flag respectively.

DP_ArithmeticLogicUnit_21363904

Case 1: Negative plus Negative with Overflow

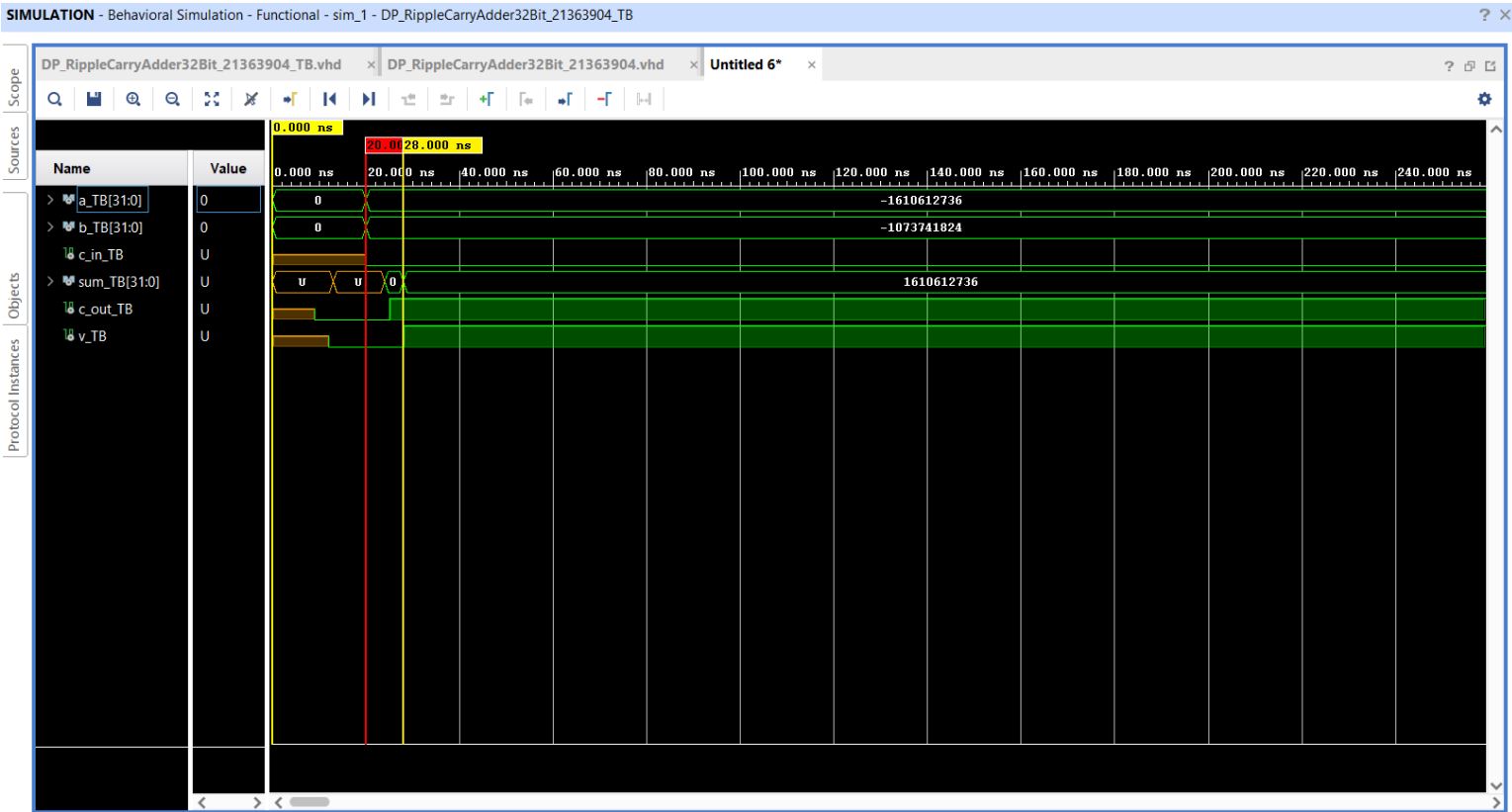


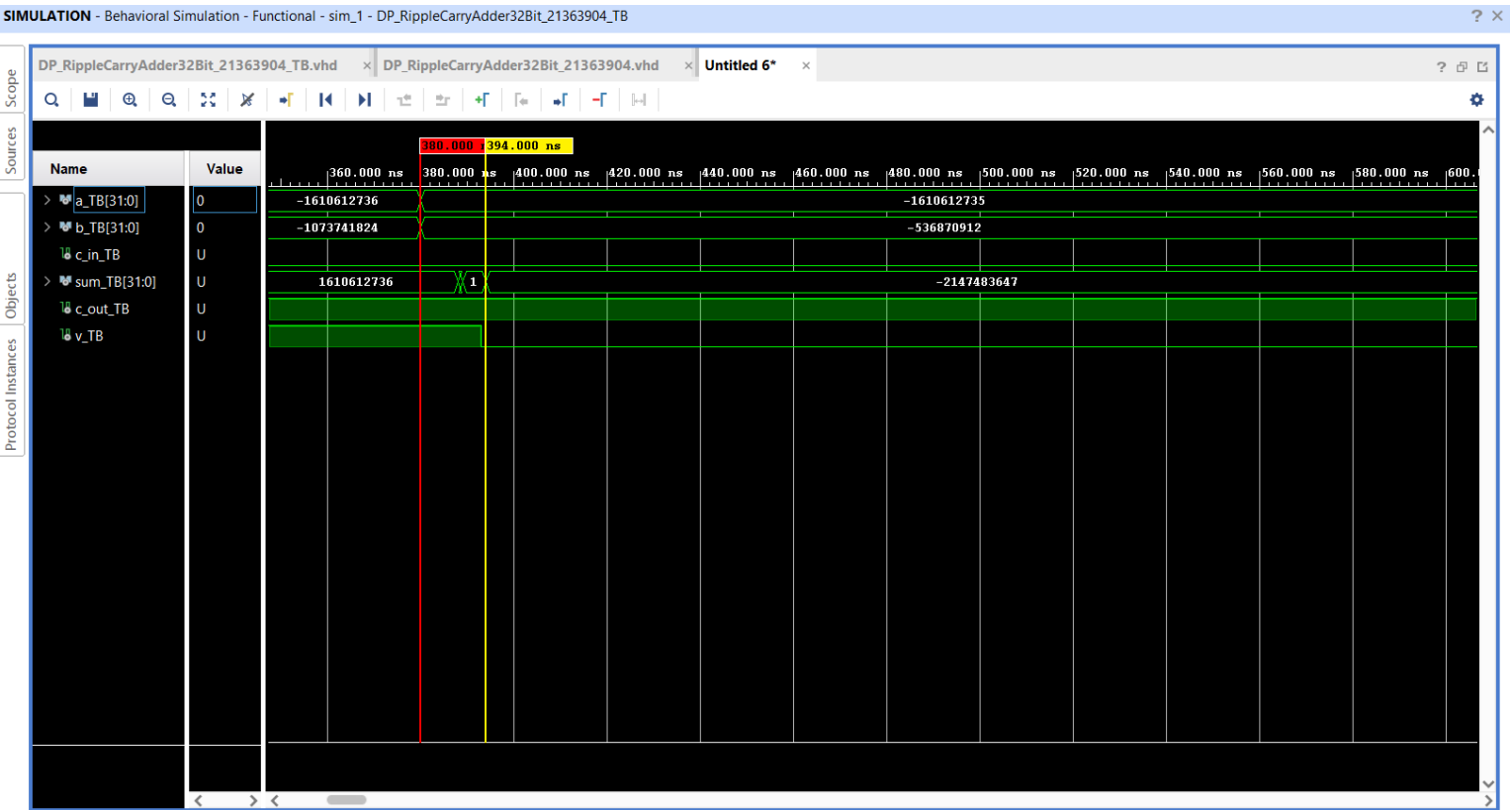Case 2: Negative plus Negative without Overflow




DP_ArithmeticLogicUnit_21363904

Case 3: Positive plus Positive with Overflow

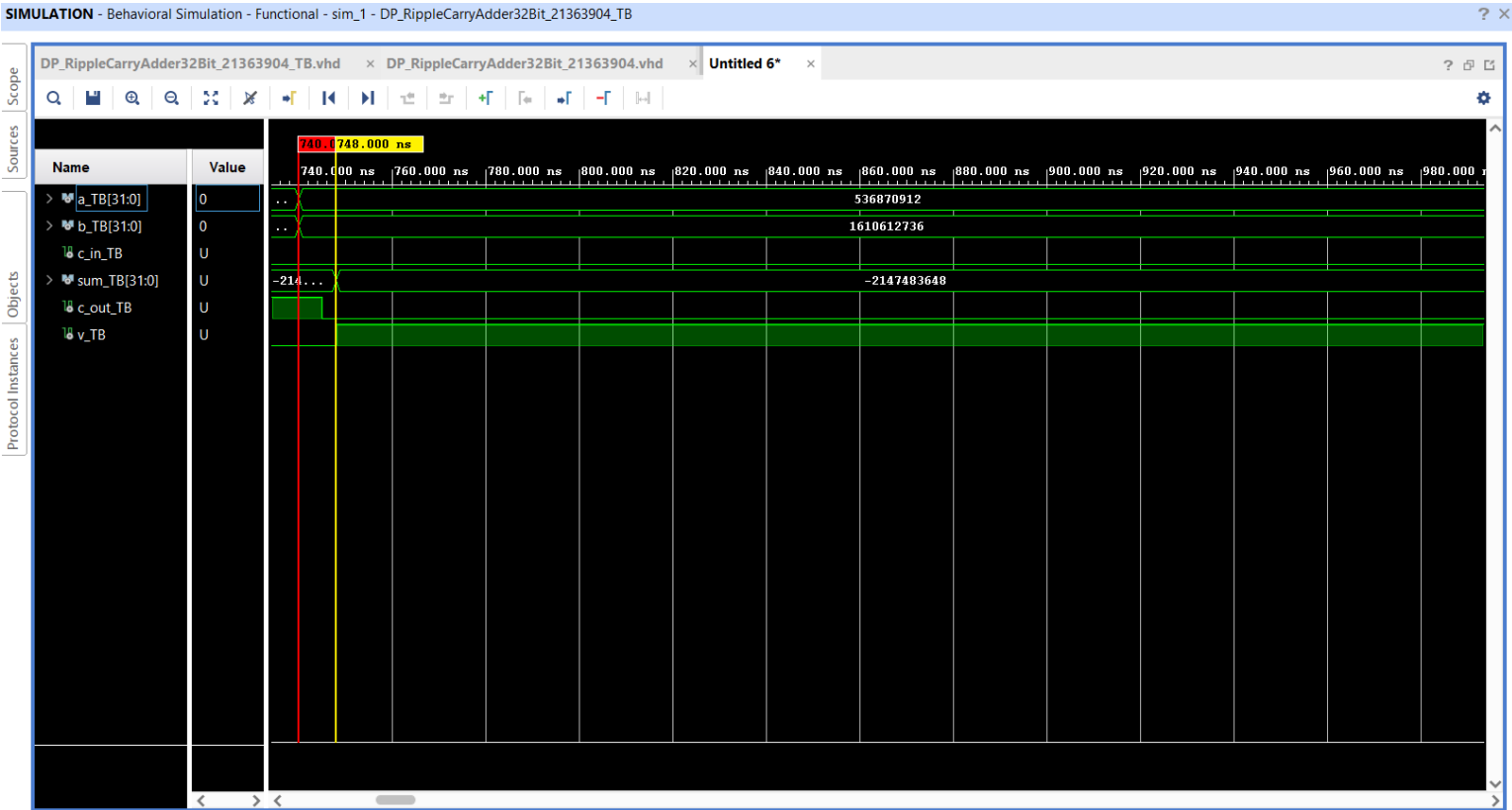


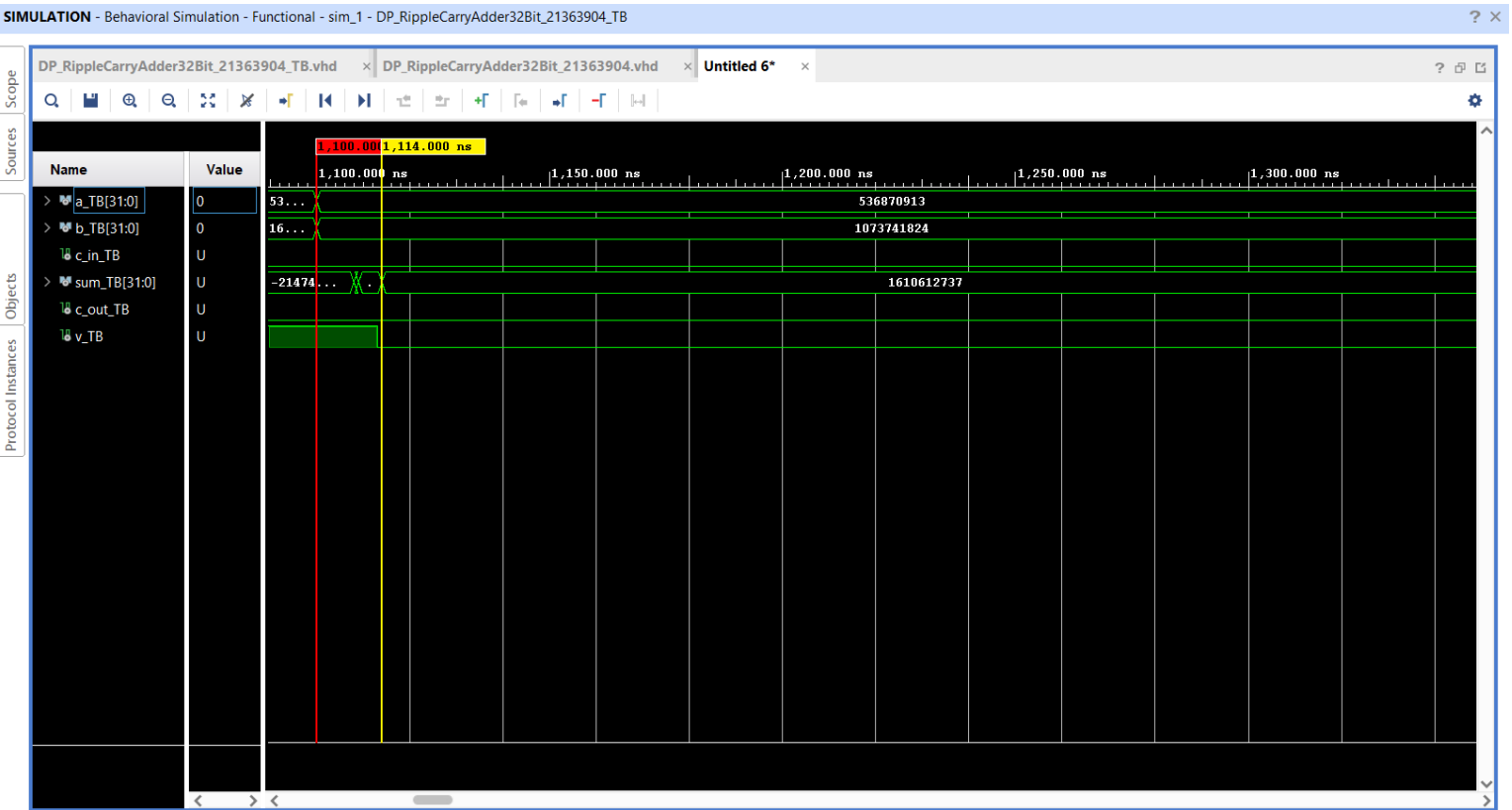Case 4: Positive plus Positive without Overflow




DP_ArithmeticLogicUnit_21363904

Case 5: Positive plus Negative without Overflow

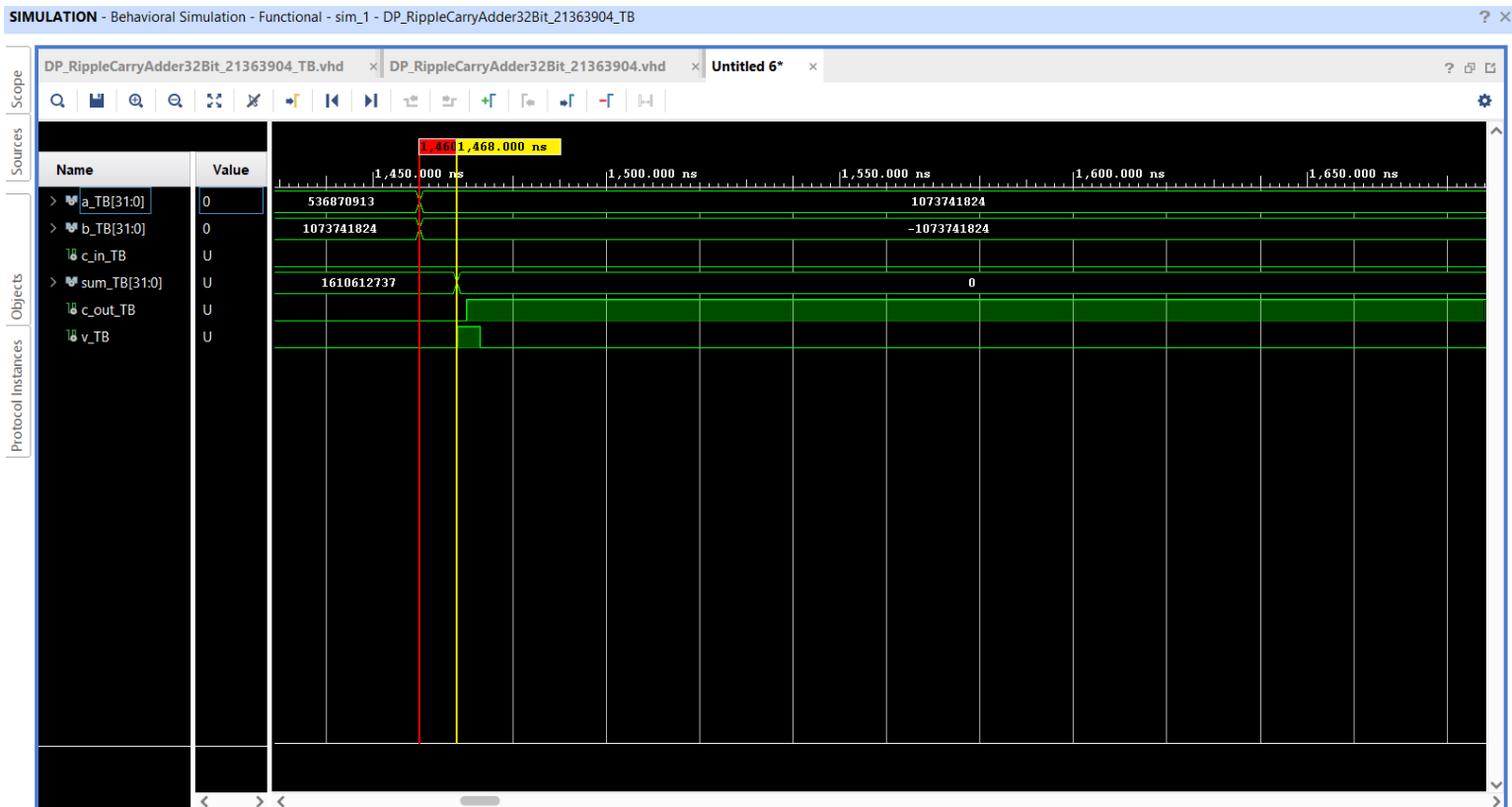


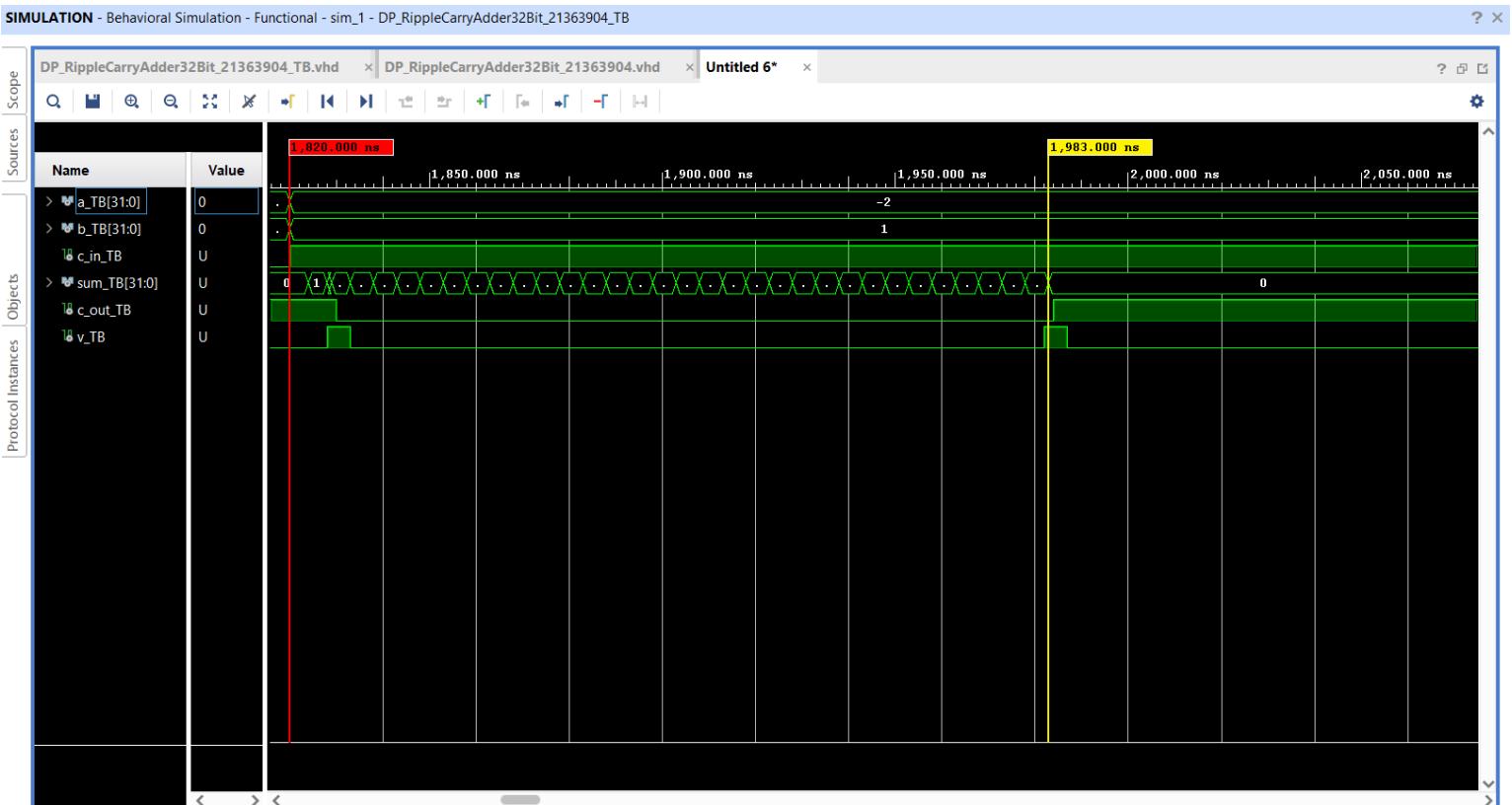Case 6: Negative plus Positive (worst-case Propagation Delay)



DP_ArithmeticLogicUnit_21363904

Case 7: Student ID – Set Carry Flag

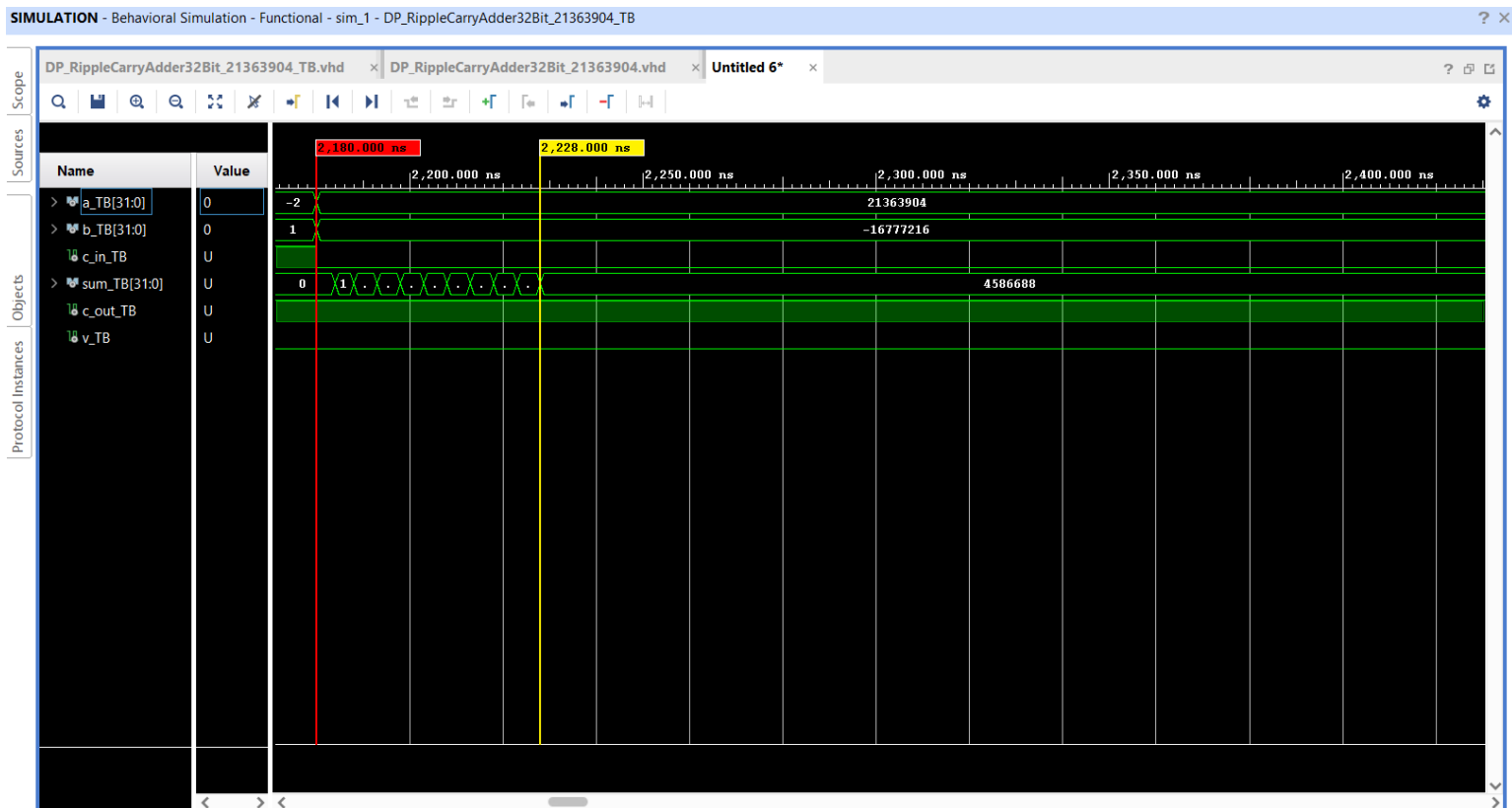

Case 8: Student ID – Set Overflow Flag

