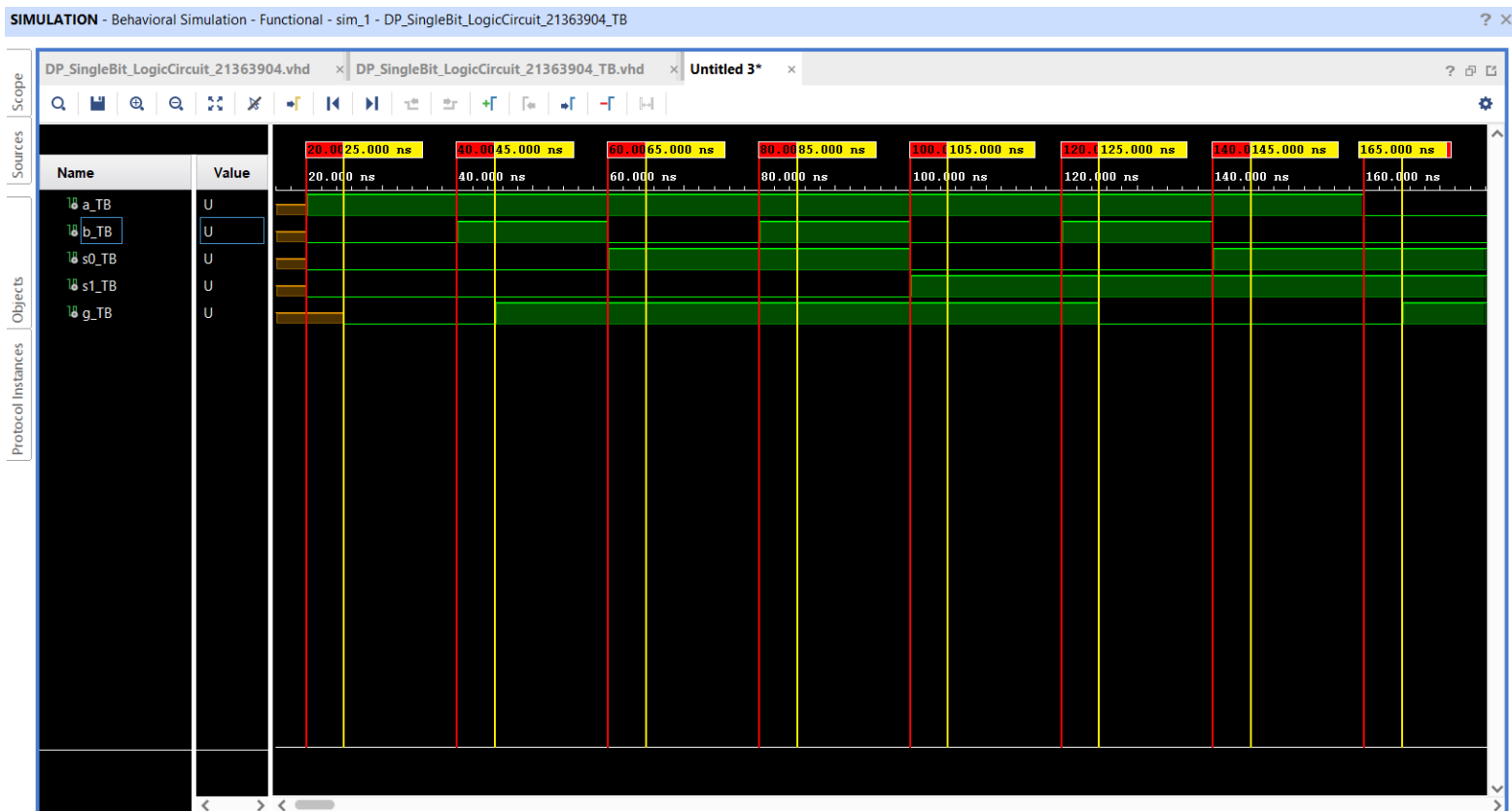


DP_SingleBit_LogicCircuit_21363904



The timing diagram for the Single Bit Logic Circuit is shown above. The **red lines** mark when the select inputs change and the **yellow lines** mark when the correct value appears at the output, after a propagation delay of 5ns. The waveform above demonstrates each of the four bitwise operations on two sets of inputs, *A* and *B*: the first three operations (*AND*, *OR* and *XOR*) are performed on 1 and 0 followed by 1 and 1, and the last operation (*NOT*) is performed on 1 followed by 0. When both selects are 0, we perform *A AND B*, when *s0* is 1, we perform *A OR B*, when *s1* is 1, we perform *A XOR B*, and when both selects are 1, we perform *NOT(A)*. We can see from the waveform that each operation yields the correct result: $1 \text{ AND } 0 = 0$, $1 \text{ AND } 1 = 1$, $1 \text{ OR } 0 = 1$, $1 \text{ OR } 1 = 1$, $1 \text{ XOR } 0 = 1$, $1 \text{ XOR } 1 = 0$, $\text{NOT}(1) = 0$, $\text{NOT}(0) = 1$.